

AVR

Embedded Systems based on AVR Diploma [AVR Diploma]

Partner with us and ignite your students'
passion for technology!

Assignment

Using 2 Relays design H-Bridge to control Direction of DC Motor.
Note : Connect the relay to transistor to achieve complete isolation



Contact Us



Thank You

Do you have any questions?